

HOMEWORK SOLUTIONS 6
Chapter 7
Frequency Response


Problems
7.1,7.3,7.4,7.5,
7.6,7.7,7.10,7.14,
7.15,7.19,7.26

Electronics II
ECGR 3132
Dr. Binkley

By:
Matt Davis
Kalyan Cherukuvada

7.1

①

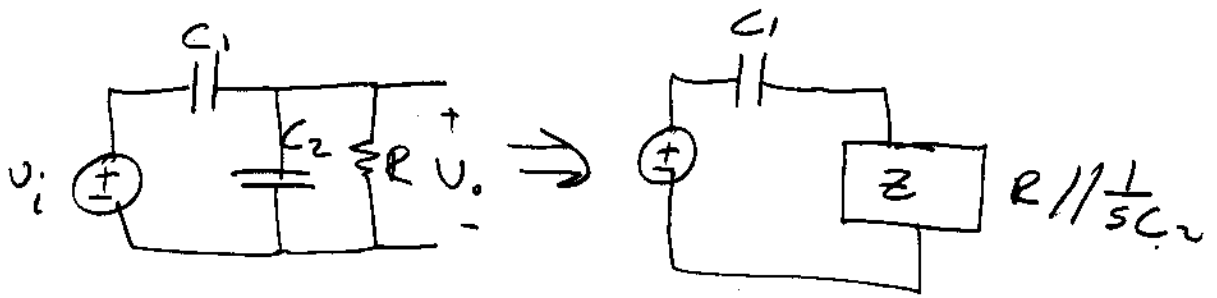

$$\frac{\frac{1}{sC_2}}{R + \frac{1}{sC_2}} = \frac{\cancel{\frac{1}{sC_2}} R}{\cancel{\frac{1}{sC_2}} (1 + sRC_2)} = \frac{R}{1 + sRC_2}$$

Once we have the impedance of the parallel combination R and C_2 we can use voltage division to find the transfer function.

$$\frac{\frac{R}{1 + sRC_2}}{\frac{R}{1 + sRC_2} + \frac{1}{sC_1}} = \frac{\frac{R}{1 + sRC_2}}{\frac{1}{sC_1} \left(R + (1 + sRC_2) \cdot \frac{1}{sC_1} \right)} = \frac{V_{out}}{V_{in}}$$

$$\frac{R}{R + \frac{1}{sC_1} + sRC_2 \left(\frac{1}{sC_1} \right)} = \frac{R}{\frac{1}{sC_1} (sRC_1 + 1 + sRC_2)}$$

$$\frac{sRC_1}{1 + sR(C_1 + C_2)} = \frac{V_{out}}{V_{in}}$$

To find the zeros set numerator equal to zero,
and solve for s

$$sRC_1 = 0 \quad s = 0$$

So zero at 0

To find the poles set denominator equal to zero,
and solve for s

$$1 + sR(C_1 + C_2) = 0$$

$$s = \frac{-1}{R(C_1 + C_2)} = \frac{-1}{100k(0.5\mu f + 0.5\mu f)} = -10 \text{ rad/sec}$$

To plot the Mag. and Phase we can rewrite
the equations

$$\frac{sRC_1}{1 + sR(C_1 + C_2)}$$

$$\omega_z = \frac{1}{RC_1} = 20 \text{ rad/sec}$$

$$\omega_p = \frac{1}{R(C_1 + C_2)} = 10 \text{ rad/sec}$$

because $s = j\omega$ we can write the equation

$$\frac{j\omega}{20}{1 + \frac{j\omega}{10}}$$

Since we know that the Bode plot starts increasing 20 dB/dec because of the zero at zero we can plug in a frequency higher than 10 rad/sec and get the max mag.

100 rad/sec was chosen

$$\frac{j \frac{100}{20}}{1 + j \frac{100}{10}} \quad \text{then } \text{Mag} = \sqrt{R^2 + I^2}$$

\swarrow real \swarrow imaginary

$$\text{Phase} = \angle \tan^{-1} \left(\frac{I}{R} \right)$$

$$\text{Mag}_{\text{max}} = \frac{\sqrt{5^2}}{\sqrt{1^2 + (10)^2}} = 0.5$$

$$20 \log 0.5 = -6 \text{ dB}$$

$$\text{Mag}_{\text{max}} = -6 \text{ dB}$$



* These are fundamental equations for electrical engineers and you should know them

* well ——— *

To find the phase just use the 3dB cutoff frequency

$$\frac{j \frac{10}{20}}{1 + j \frac{10}{10}} = \frac{\angle \tan^{-1} \frac{1}{0}}{\angle \tan^{-1} (1)} = \frac{\angle 90}{\angle 45} = \angle -45^\circ$$

So our Bode plot will look like this

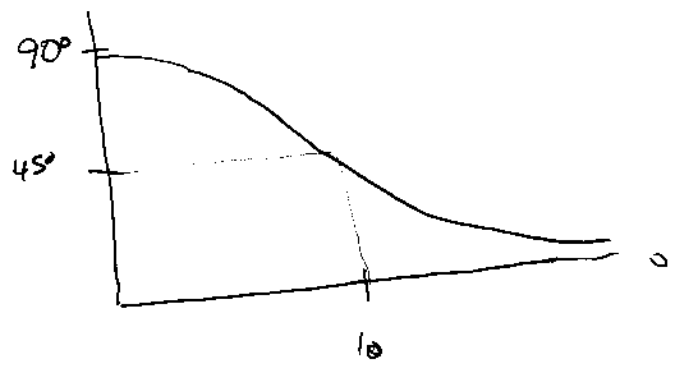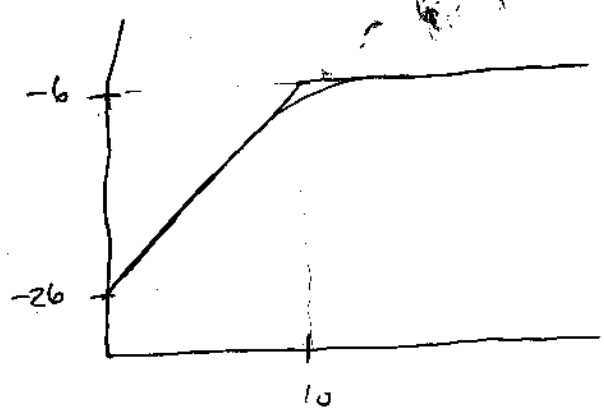

7.3) There are three possible situations.

- ① Both are Low pass LP
- ② Both are High pass HP
- ③ one is LP and the other is LP

① Both are Low pass, Because they are equal they will have the same transfer function.

$$T_1(s) = T_2(s) = \frac{1}{1 + j\frac{\omega}{\omega_p}} = \frac{1}{1 + j\frac{\omega}{100}}$$

To find the total gain we have to multiply $T_1(s)$ and $T_2(s)$ together.

$$T(s) = T_1(s)T_2(s) = \left(\frac{1}{1 + j\frac{\omega}{100}} \right)^2$$

Now take the mag and plug in frequency

$$|T(s)| = \left[\frac{1}{\sqrt{1 + \left(\frac{10}{100}\right)^2}} \right]^2 = 0.99 @ 10 \text{ rads/sec}$$

$$|T(s)| = \left[\frac{1}{\sqrt{1 + \left(\frac{100}{100}\right)^2}} \right]^2 = 0.5 @ 100 \text{ rads/sec}$$

$$|T(s)| = \left[\frac{1}{\sqrt{1 + \left(\frac{1000}{10}\right)^2}} \right]^2 = 0.01 @ 1000 \text{ rads/sec}$$

② Both are HP

$$T_1(s) = T_2(s) = \frac{s}{s+w} = \frac{1}{1+\frac{w}{s}} = \frac{1}{1+\frac{100}{s}}$$

$$T(s) = \left(\frac{1}{1+\frac{100}{j\omega}} \right)^2 = \left(\frac{1}{1-j\frac{100}{\omega}} \right)^2$$

$$|T(s)| = \left[\frac{1}{\sqrt{1+\left(\frac{100}{\omega}\right)^2}} \right]^2 = 0.01 @ 10 \text{ rad/sec}$$

$$T(s) = \left[\frac{1}{\sqrt{1+\left(\frac{100}{100}\right)^2}} \right]^2 = 0.5 @ 100 \text{ rad/sec}$$

$$T(s) = \left[\frac{1}{\sqrt{1+\left(\frac{100}{1000}\right)^2}} \right]^2 = 0.99 @ 1000 \text{ rad/sec}$$

③ one LP and other HP

$$T_1(s) = \frac{1}{1+\frac{s}{100}} \quad T_2(s) = \frac{1}{1+\frac{100}{s}}$$

$$T(s) = \left(\frac{1}{1+\frac{s}{100}} \right) \left(\frac{1}{1+\frac{100}{s}} \right) = \left[\frac{1}{1+j\frac{\omega}{100}} \right] \left[\frac{1}{1-j\frac{100}{\omega}} \right]$$

$$|T(s)| = \left[\frac{1}{\sqrt{1+\left(\frac{10}{100}\right)^2}} \right] \left[\frac{1}{\sqrt{1+\left(\frac{100}{10}\right)^2}} \right] = 0.1 @ 10 \text{ rad/sec}$$

$$T(s) = \left[\frac{1}{\sqrt{1+\left(\frac{100}{100}\right)^2}} \right] \left[\frac{1}{\sqrt{1+\left(\frac{100}{100}\right)^2}} \right] = 0.5 @ 100 \text{ rad/sec}$$

$$T(s) = \left[\frac{1}{\sqrt{1+\left(\frac{1000}{100}\right)^2}} \right] \left[\frac{1}{\sqrt{1+\left(\frac{100}{1000}\right)^2}} \right] = 0.1 @ 1000 \text{ rad/sec}$$

7.4

$$T(s) = \frac{a_1 s}{s + \omega_0}$$

High frequency gain = $a_1 = 10 \text{ V/V}$

$$\therefore a_1 = 10$$

$$\text{At } s = j2\pi(10), \quad |T| = 1$$

$$\text{Thus } \left. \frac{a_1}{\sqrt{1 + \left(\frac{\omega_0}{\omega}\right)^2}} \right|_{\omega = 2\pi(10)} = 1$$


$$\Rightarrow \sqrt{1 + \left(\frac{\omega_0}{\omega}\right)^2} = a_1 = 10$$

$$\omega_0 = 2\pi(10)(\sqrt{99})$$

$$= 625 \text{ rad/s}$$

$$(f_0 \approx 100 \text{ Hz})$$

75

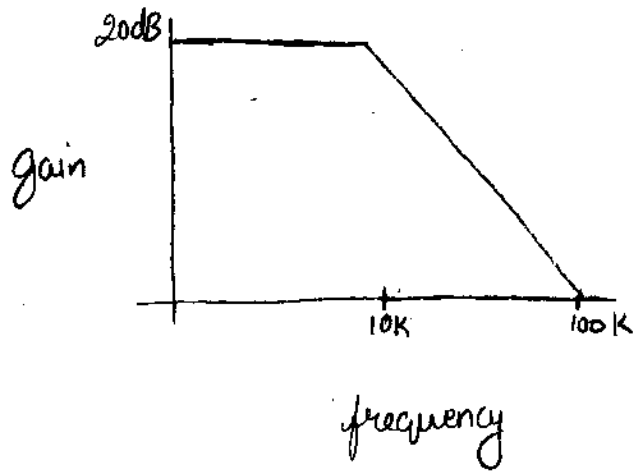

Since we decrease by 20 dB at a pole and we know that 100K is 0 dB and low frequency is 20 dB this leads to 10 KHz corner frequency.

$$T(s) = \frac{10}{1 + \frac{s}{2\pi(10^4)}}$$

$$|T(j\omega)| = \frac{10}{\sqrt{1 + (\omega/2\pi(10^4))^2}}$$

$$= \frac{10}{\sqrt{1 + (f/10^4)^2}}$$

$$20 \log |T| = 20 - 10 \log \left(1 + \frac{f^2}{10^8} \right)$$

Since given gain = 19 dB

$$19 = 20 - 10 \log \left(1 + \frac{f^2}{10^8} \right)$$

$$1 + \frac{f^2}{10^8} = 10^{0.1}$$

$$f = 10^4 \sqrt{10^{0.1} - 1}$$

$$= 5088.5 \text{ Hz}$$

$$\phi = -\tan^{-1} \left(\frac{f}{10^4} \right)$$

$$-6^\circ = -\tan^{-1} \left(\frac{f}{10^4} \right)$$

$$f = 1051 \text{ Hz}$$

7.6


Other poles must be at $-7-j10$ (Complex conjugate)

Other zeros must be at $-1+j20$ (Complex conjugate)

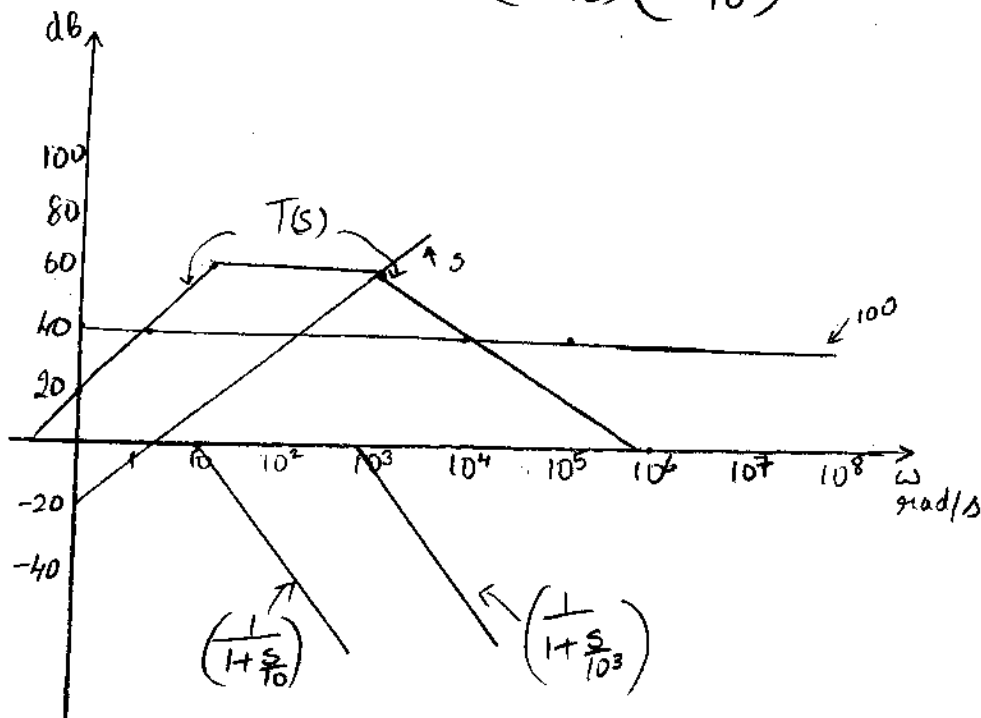7.7

Convenient form for constructing Bode Plots

$$T(s) = \frac{100s}{\left(1 + \frac{s}{10}\right)\left(1 + \frac{s}{10^3}\right)}$$



From Bode Plot:

ω	1	10	10^2	10^3	10^4	10^5
$ T $	40	60	60	60	40	20

From Transfer function:-

Gain at 10 rad/s

$$|T(j10)| = \frac{100 \times 10}{\sqrt{1 \times 1} \sqrt{1 + (0.01)^2}} \approx \frac{1000}{\sqrt{2}}$$

$$\Rightarrow 57 \text{ dB}$$


Gain at 10^3 rad/s

$$|T(j10^3)| = \frac{100 \times 10^3}{\sqrt{1 \times 10^4} \sqrt{1 \times 1}} \approx \frac{1000}{\sqrt{2}}$$

$$\Rightarrow 57 \text{ dB}$$

$$7.10) \quad T(s) = \frac{10^4 (1 + s/10^5)}{(1 + s/10^3)(1 + s/10^4)}$$

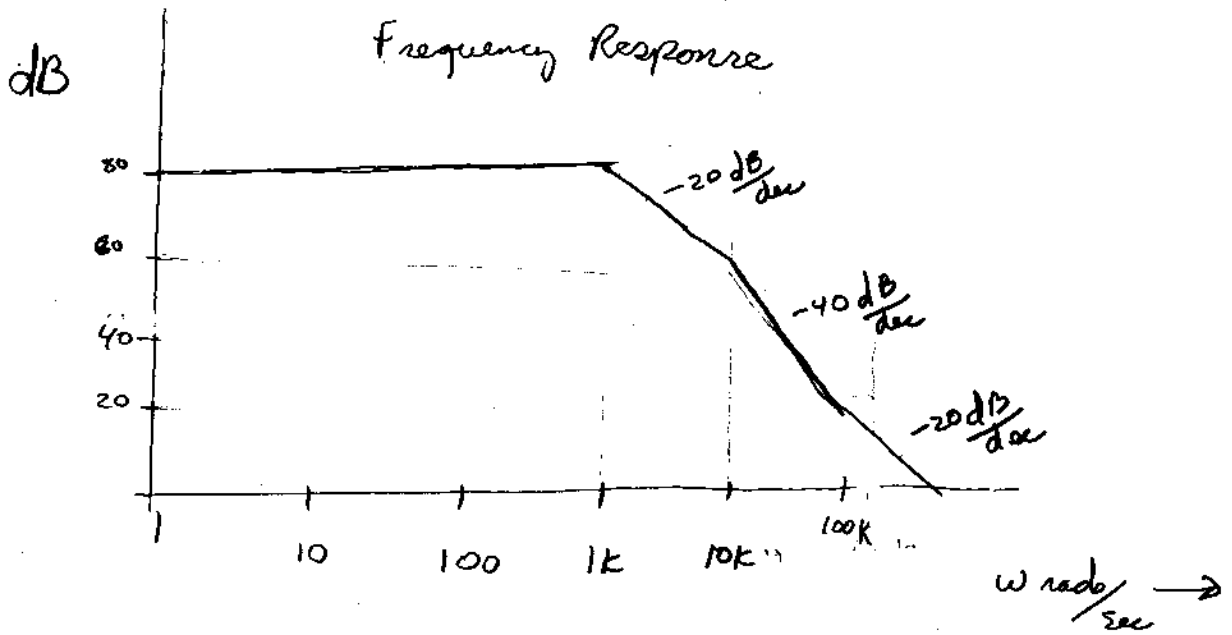Since max gain will be 10^4 this is where we start



$$A_v = 10^4 = 80 \text{ dB}$$

The first and dominant pole is at 1k


$$1 + \frac{s}{10^3} \leftarrow w_{p1}$$

Next pole is at 10k


$$1 + \frac{s}{10^4} \leftarrow w_{p2}$$

Zero is at 100k

$$1 + \frac{s}{10^5} \leftarrow w_{z1}$$

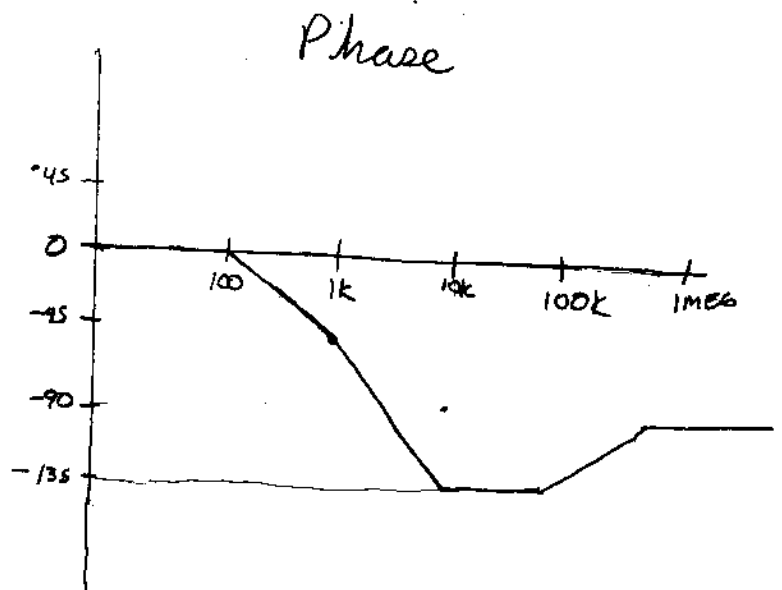

7.14)

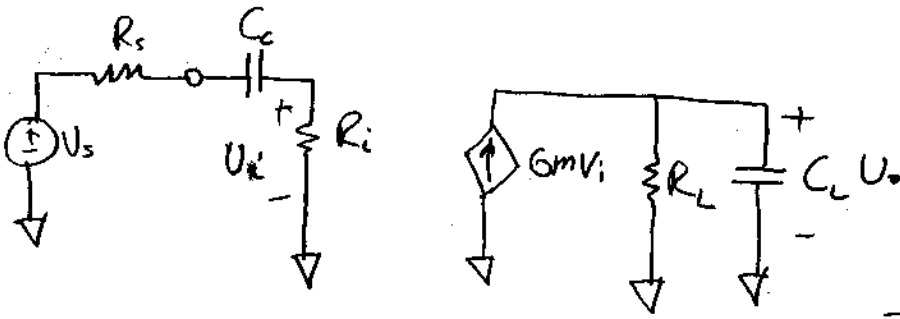

$$Z_L = R_L \parallel \frac{1}{sC_L}$$

$$a) \quad V_{out} = G_m V_i Z_L \quad \frac{V_{out}}{V_i} = G_m Z_L$$

$$V_i = V_s \frac{R_i}{R_s + \frac{1}{sC_c} + R_i} = V_s \frac{s R_i C_c}{1 + s(R_i + R_s)C_c}$$

$$\frac{V_i}{V_s} = \frac{s R_i C_c}{1 + s(R_i + R_s)C_c}$$

$$\frac{U_o}{V_s} = G_m Z_L \left(\frac{s R_i C_c}{1 + s(R_i + R_s)C_c} \right)$$

$$Z_L = \frac{1}{\frac{1}{R_L} + sC_L} = \frac{R_L}{1 + sR_L C_L}$$

$$\frac{U_o}{V_s} = G_m \left(\frac{R_L}{1 + sR_L C_L} \right) \left(\frac{s R_i C_c}{1 + s(R_i + R_s)C_c} \right)$$

To find A_m short all caps.

$$b) \quad A_m = \left(\frac{R_i}{R_i + R_s} \right) (G_m R_L)$$

$$F_L = \frac{s}{s + \frac{1}{C_c(R_s + R_i)}}$$

$$F_H = \frac{1}{1 + sR_L C_L}$$

$$A_m = 20 \text{ dB} \quad \Rightarrow \quad 20 \log(A_m) = 20 \text{ dB}$$

$$A_m = 10 \frac{V}{V}$$

Since

$$A_m = \left(\frac{R_L}{R_L + R_S} \right) (G_m R_L)$$

$$10 = \left(\frac{100 \text{ k}}{100 \text{ k} + 20 \text{ k}} \right) (G_m (10 \text{ k}))$$

$$G_m = 1.2 \frac{\text{mA}}{\text{V}}$$

d)

$$f_L \leq 10 \text{ Hz}$$

$$f_L = \frac{1}{2\pi C_c (R_S + R_i)} \quad \Rightarrow \quad C_c = \frac{1}{2\pi f_L (R_S + R_i)}$$

$$C_c = \frac{1}{2\pi (10) (20 \text{ k} + 100 \text{ k})} = 0.13 \mu\text{F}$$

$$C_{c \text{ min}} = 0.13 \mu\text{F}$$

e)

$$f_H > 1 \text{ MHz}$$

$$f_H = \frac{1}{2\pi R_L C_L} \quad \Rightarrow \quad C_L = \frac{1}{2\pi R_L f_H}$$


$$C_L = \frac{1}{2\pi (10 \text{ k})(1 \text{ MHz})} = 15.9 \text{ pF} \approx 16 \text{ pF}$$

$$C_L = 16 \text{ pF}$$

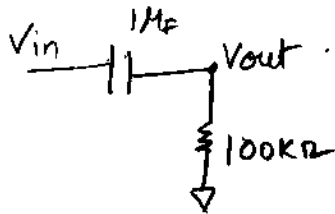7.15.

$$A_M = 100 \text{ V/V} \text{ (Given)}$$

$F_L(s)$ is determined from the input circuit




By voltage division:

$$V_{out} = V_{in} \left(\frac{R}{R + \frac{1}{sC}} \right)$$

$$\frac{V_{out}}{V_{in}} = \frac{10^5}{10^5 + \frac{1}{5 \times 10^{-6}}}$$

$$= \frac{s}{s + 10}$$

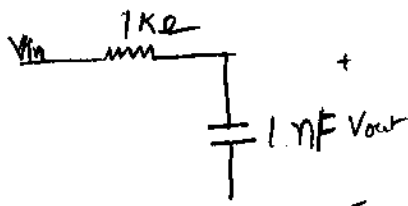$F_H(s)$ is determined from the output circuit



$$V_{out} = V_{in} \left(\frac{\frac{1}{sC}}{R + \frac{1}{sC}} \right)$$

$$\frac{V_{out}}{V_{in}} = \frac{\frac{1}{s10^{-9}}}{R + \frac{1}{s10^{-9}}}$$

$$= \frac{1}{1 + \frac{s}{10^6}}$$

$$\omega_L(s) = 10 \text{ rad/s}$$

$$\omega_H(s) = 10^6 \text{ rad/s}$$

7.19.

Low Frequency Response

By dominant pole approximation.

$$f_L \approx 90 \text{ Hz}$$

By square root sum of squares.

$$f_L = \sqrt{10^2 + 20^2 + 90^2 - 2 \times 15^2}$$
$$= 90.8 \text{ Hz}$$

High Frequency response:

By dominant Pole approximation $f_H = 15 \text{ KHz}$.

By square root sum of squares

$$f_H = \sqrt{\left(\frac{1}{15}\right)^2 + \left(\frac{1}{40}\right)^2}$$
$$= 14 \text{ KHz}.$$

7.26)

$$R = 100k$$

$$R_{in} = 1.2 \text{ MEG}$$

$$g_m = 2 \text{ mA/V}$$

$$R'_L = 12k$$

$$C_{gs} = C_{gd} = 1 \text{ pF}$$

$$A_m = -22.2 \frac{\text{V}}{\text{V}}$$

$$f_{-3dB} =$$

$$A_m = \frac{V_o}{V_{in}} = \frac{-R_{in}}{R_{in} + R} (g_m R'_L)$$

$$= \left(\frac{-1.2 \text{ MEG}}{1.2 \text{ MEG} + 100k} \right) \left(2 \text{ mA/V} (12k) \right)$$

$$= -22.2 \frac{\text{V}}{\text{V}}$$

$$R_{gs} = R_{in} // R = 1.2 \text{ MEG} // 100k = 92.3k$$

$$\tau_{gs} = C_{gs} R_{gs} = (1 \text{ pF}) (92.3k) = 92.3 \text{ ns}$$

$$R_{gd} = R' + R'_L + g_m R_L R' \quad R' = R_{in} // R = 92.3k$$

$$= 92.3k + 12k + 2 \text{ mA} \cdot 92.3k = 2.32 \text{ MEG}$$

$$\tau_{gd} = C_{gd} R_{gd} = 1 \text{ pF} (2.32 \text{ MEG}) = 2320 \text{ ns}$$

$$\omega_H = \frac{1}{\tau_{gs} + \tau_{gd}} = \frac{1}{92.3 \text{ ns} + 2320 \text{ ns}} = 414.5 \text{ k rad/sec}$$

$$f_H = \frac{\omega_H}{2\pi} = \frac{414.5 \text{ k rad/sec}}{2\pi} = 66 \text{ kHz}$$